
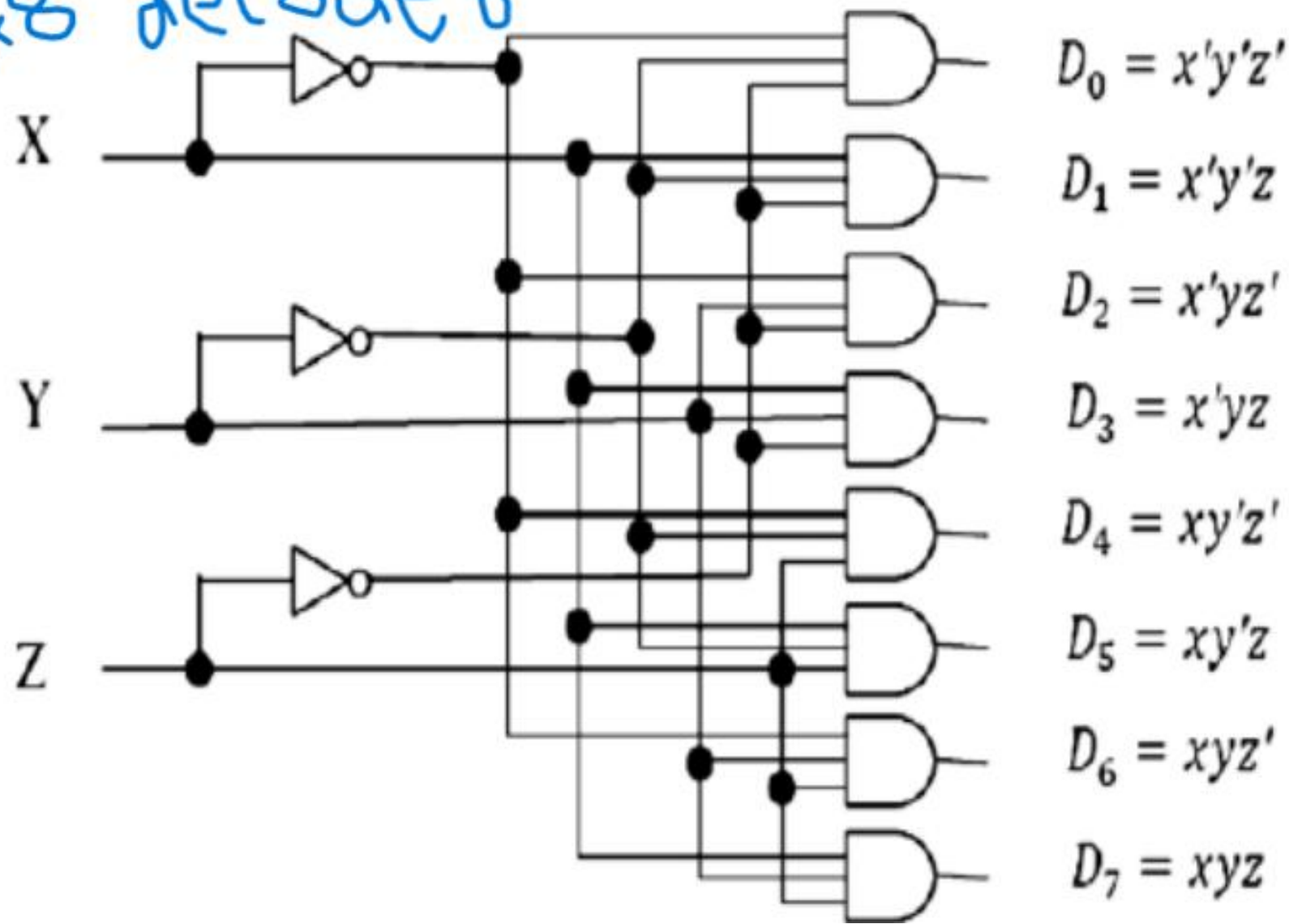


3x8 decoder

 


Encoders



*Only one
LOW input
at a time


2-4 decoder with enable

 


Implementation 2-to-4 decoder with enable

Decimal value	Enable	Inputs		Outputs			
	E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
	0	X	X	0	0	0	0
0	1	0	0	1	0	0	0
1	1	0	1	0	1	0	0
2	1	1	0	0	0	1	0
3	1	1	1	0	0	0	1

3 x 8 decoder
using
2 x 4
decoder

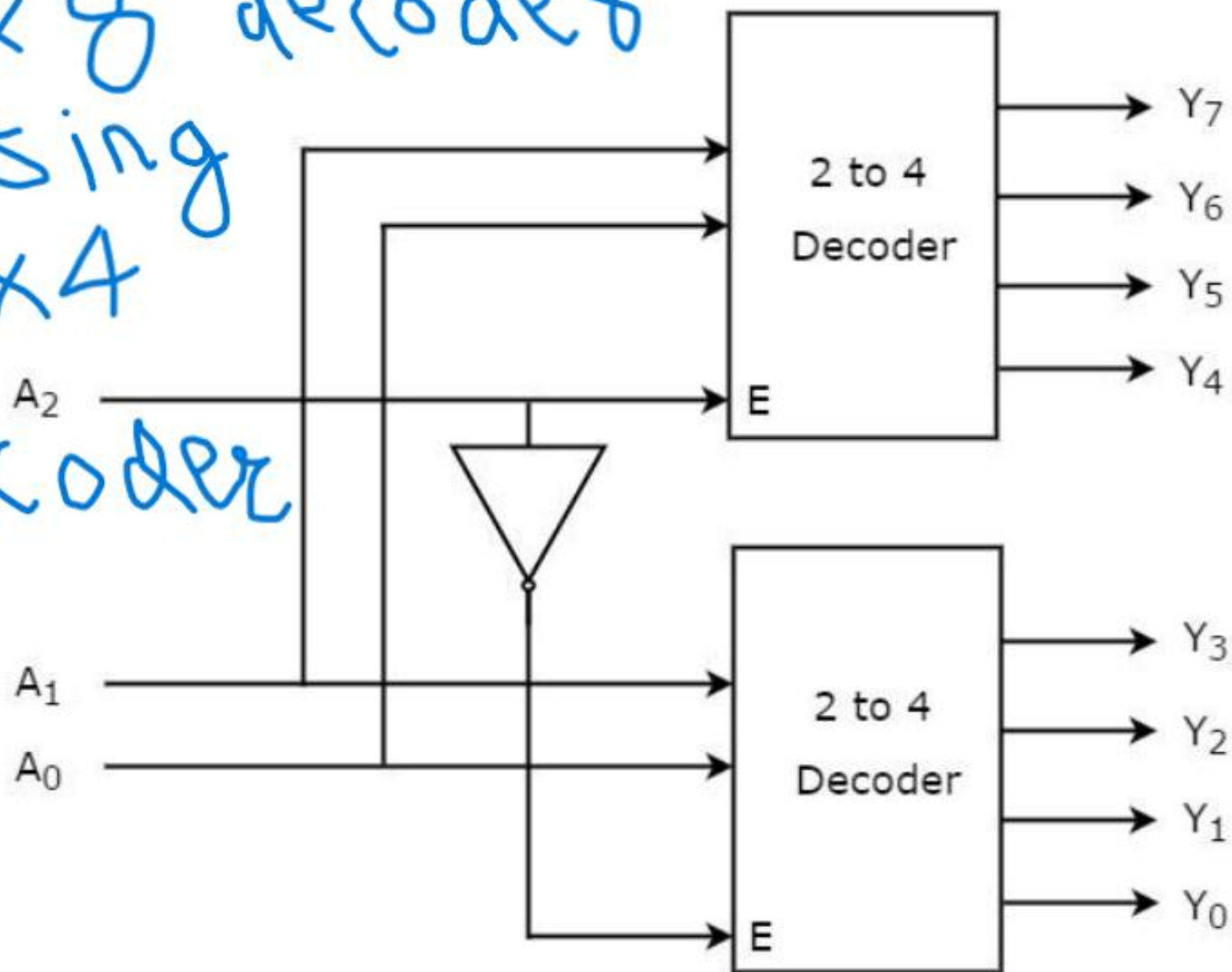


4 to 16 decoder using 2 to 4 decoder

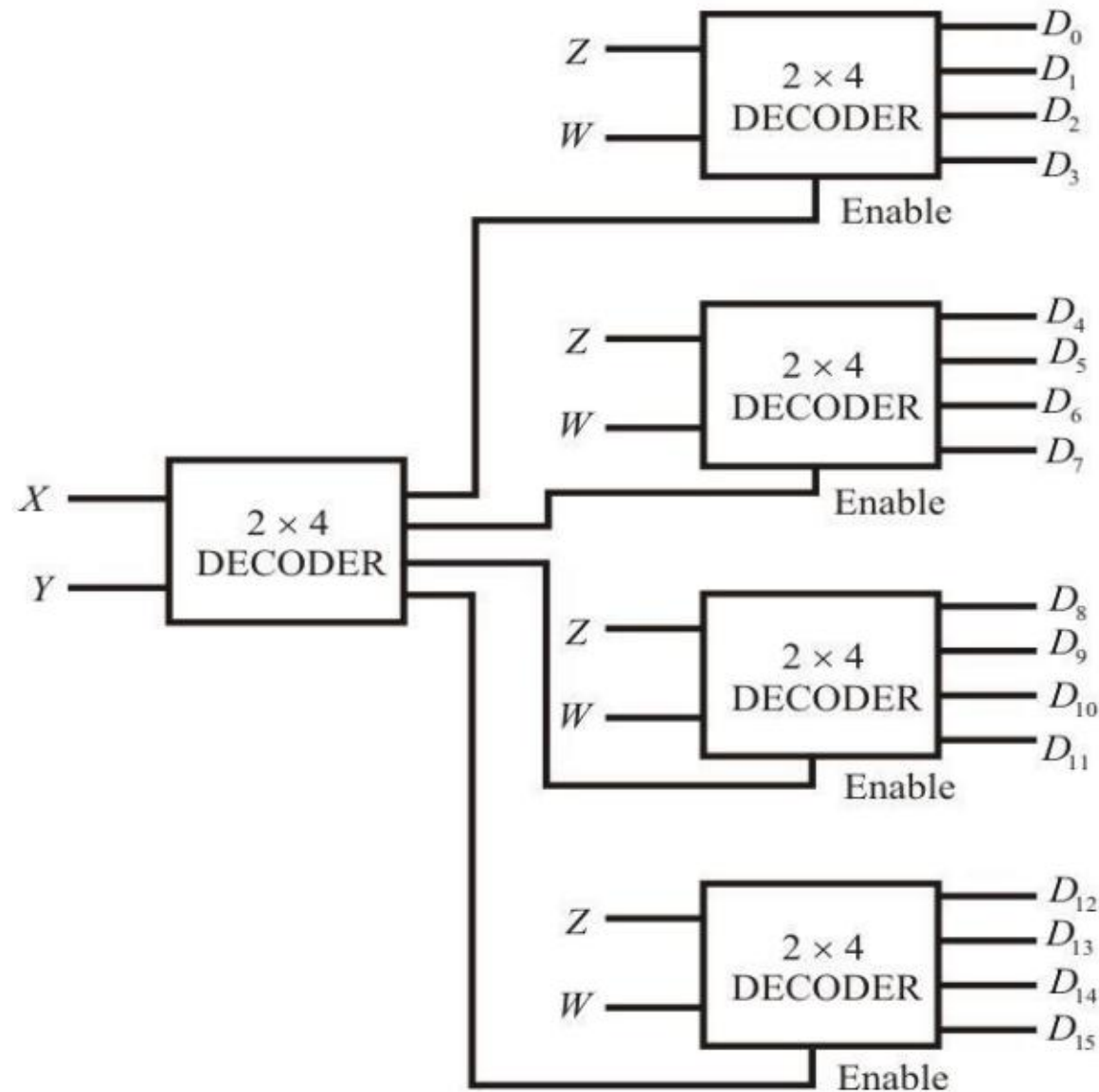


Multiplexer

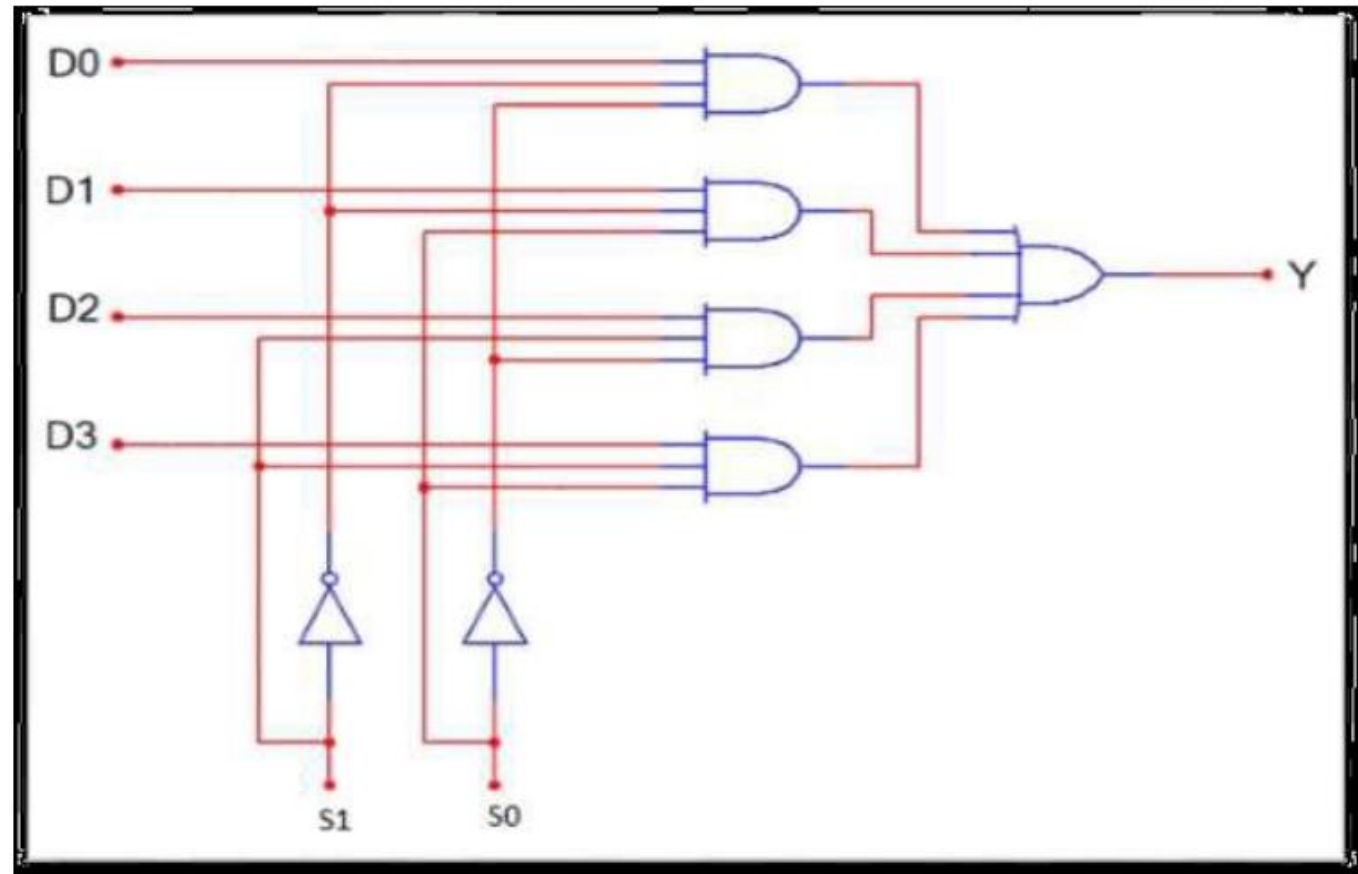- The logical level applied to the S input determines which AND gate its data input passes through the OR gate to the output.
- The output, $Y = S_1'S_0'D_0 + S_1'S_0D_1 + S_1S_0'D_2 + S_1S_0D_3$



Multiplexer


Selection Lines		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

Demultiplexer

 1-4 Demultiplexer : The 1-to-4 demultiplexer comprises 1- input bit, 4-output bits, and control bits. The 1x4 demultiplexer circuit diagram is shown below.




Selection Inputs		Outputs			
S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 


1X4 Demux

3 outputs.


1X8 Demux

 

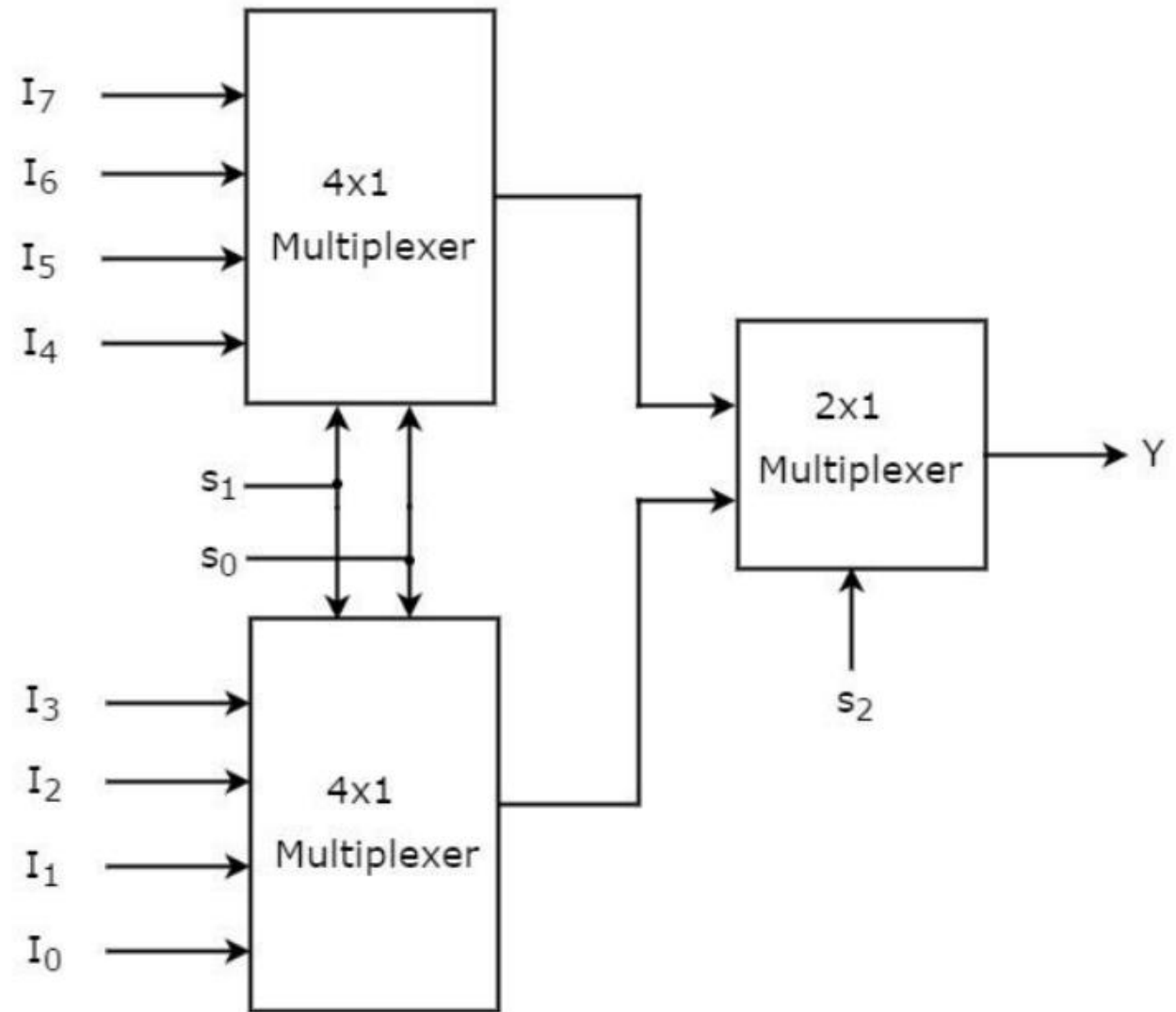
Implement 8x1 Multiplexer using 4x1 Multiplexers and 2x1 Multiplexer.



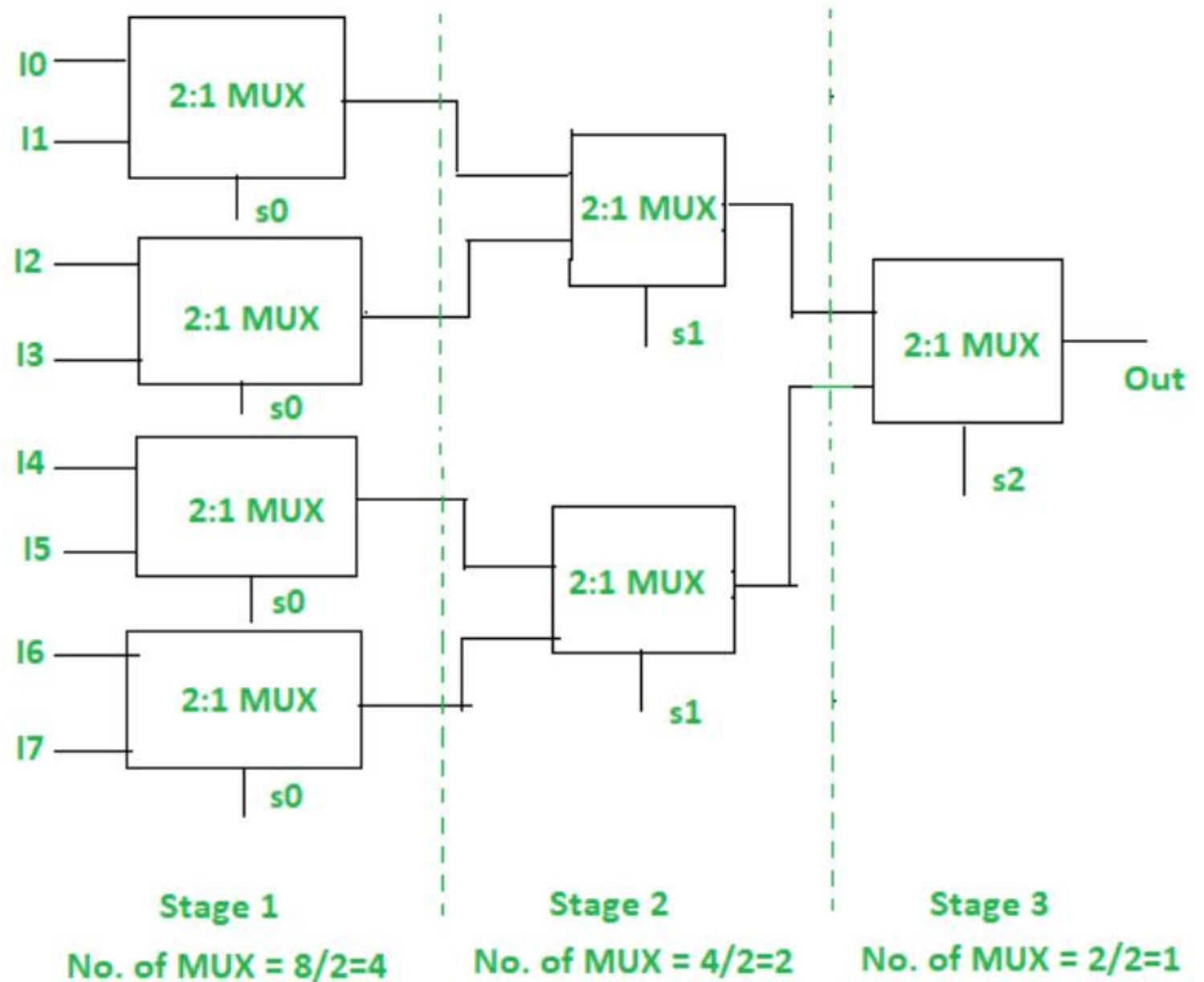Implement 8x1 Multiplexer using 2x1 Multiplexer.




16x1 Multiplexer

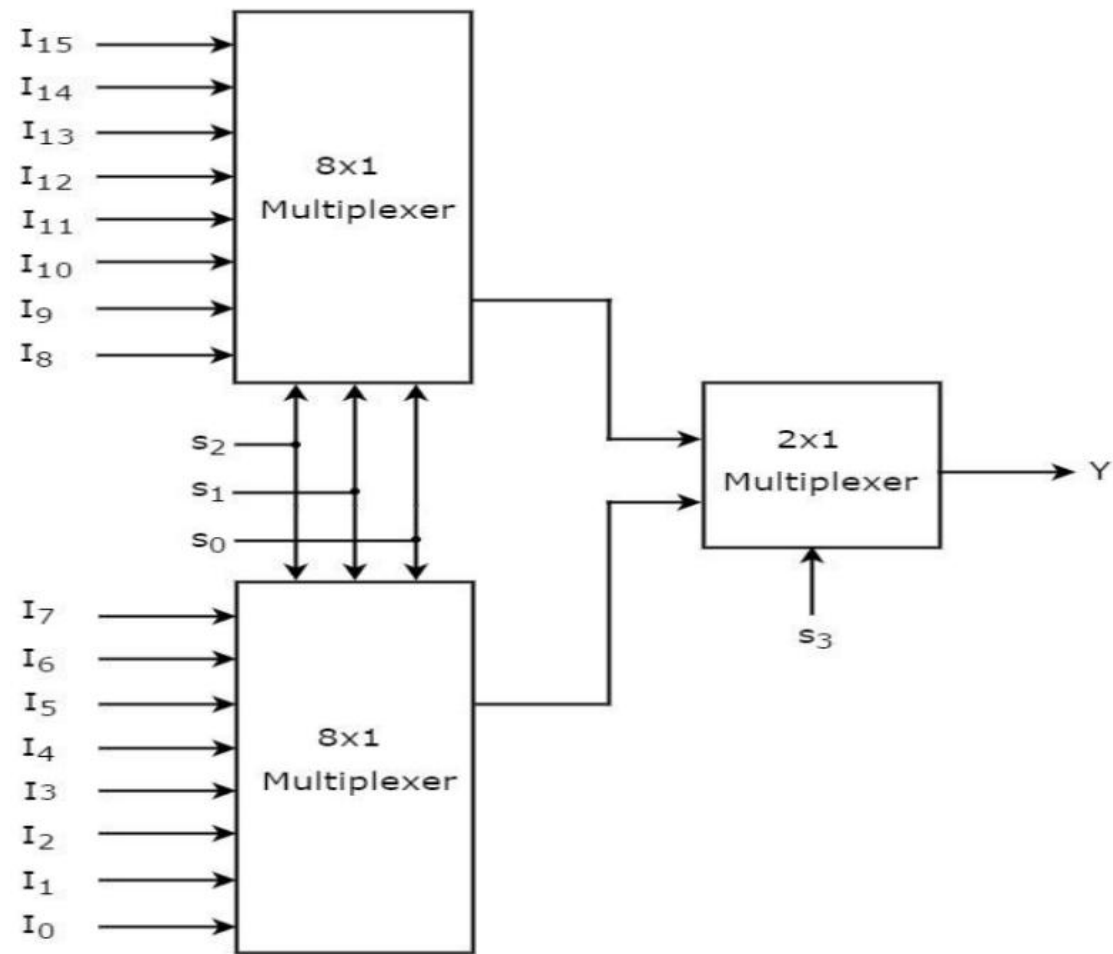

Selection Inputs				Output
S3	S2	S1	S0	Y
0	0	0	0	I_0
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7
1	0	0	0	I_8
1	0	0	1	I_9
1	0	1	0	I_{10}
1	0	1	1	I_{11}
1	1	0	0	I_{12}
1	1	0	1	I_{13}
1	1	1	0	I_{14}
1	1	1	1	I_{15}


Even Parity Generator

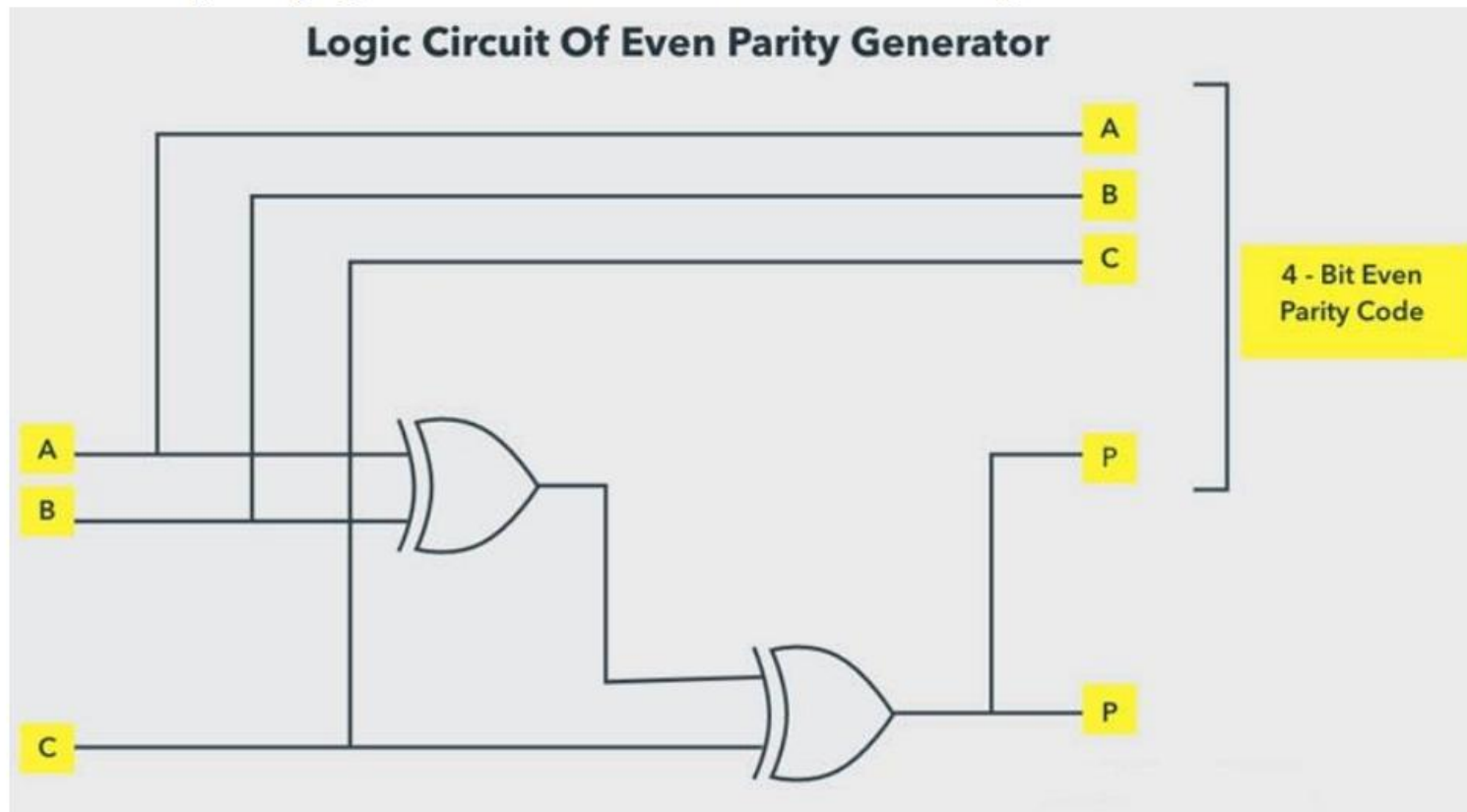- The above expression can be implemented by using two Ex-OR gates. The logic diagram of even parity generator with two Ex – OR gates is shown below.




Odd Parity Generator

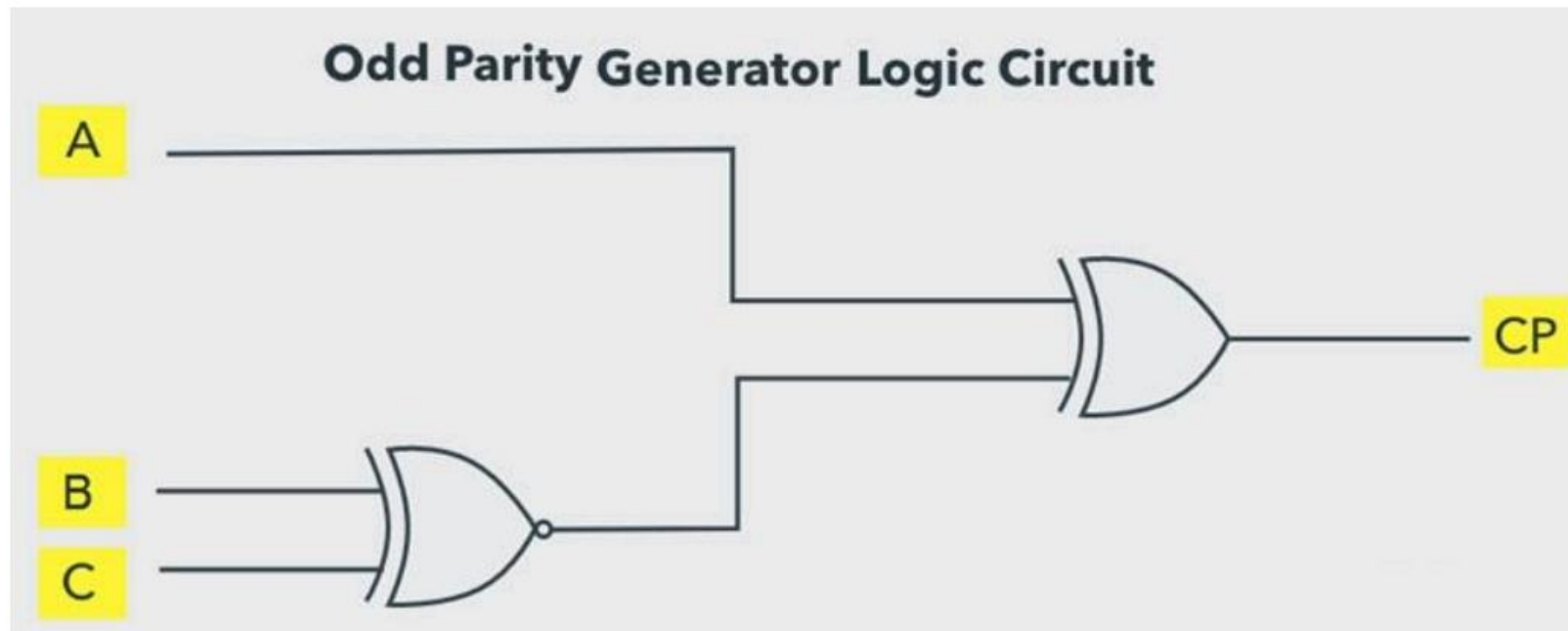- The output parity bit expression for this generator circuit is obtained as
- $P = A \oplus (B \oplus C)'$




Even Parity Checker

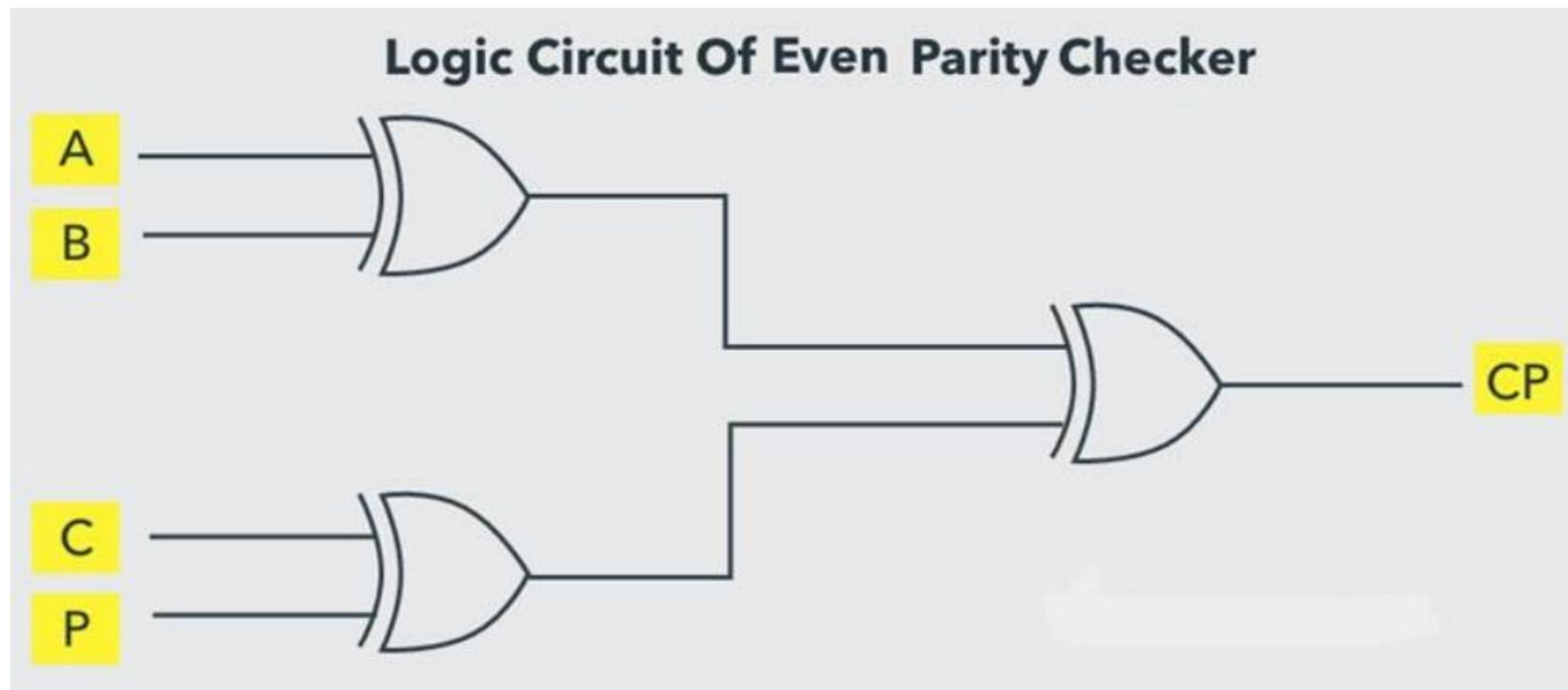- The above logic expression for the even parity checker can be implemented by using three Ex-OR gates as shown in figure. If the received message consists of five bits, then one more Ex-OR gate is required for the even parity checking.




Odd Parity Checker

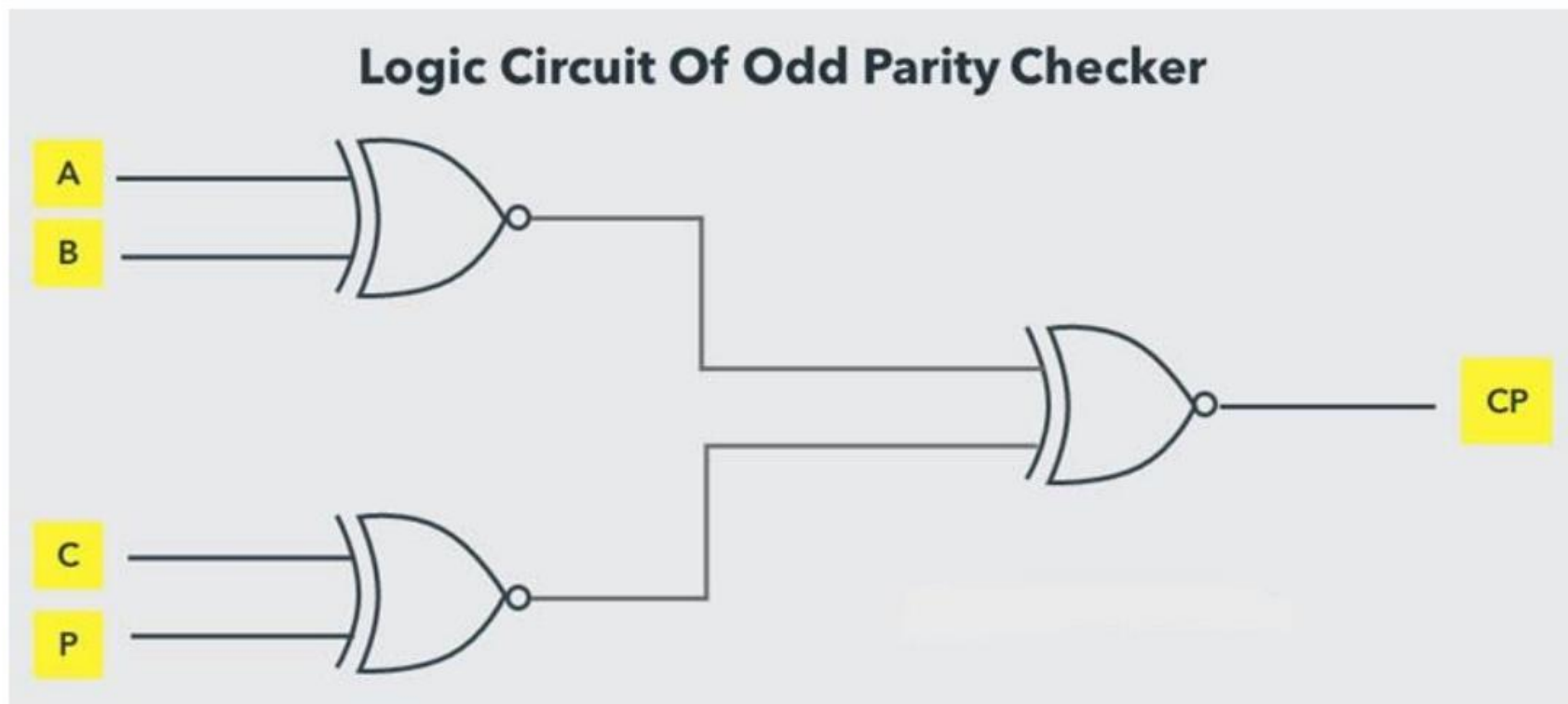- After simplification, the final expression for the PEC is obtained as
$$PEC = (A \text{ Ex-NOR } B) \text{ Ex-NOR } (C \text{ Ex-NOR } P)$$




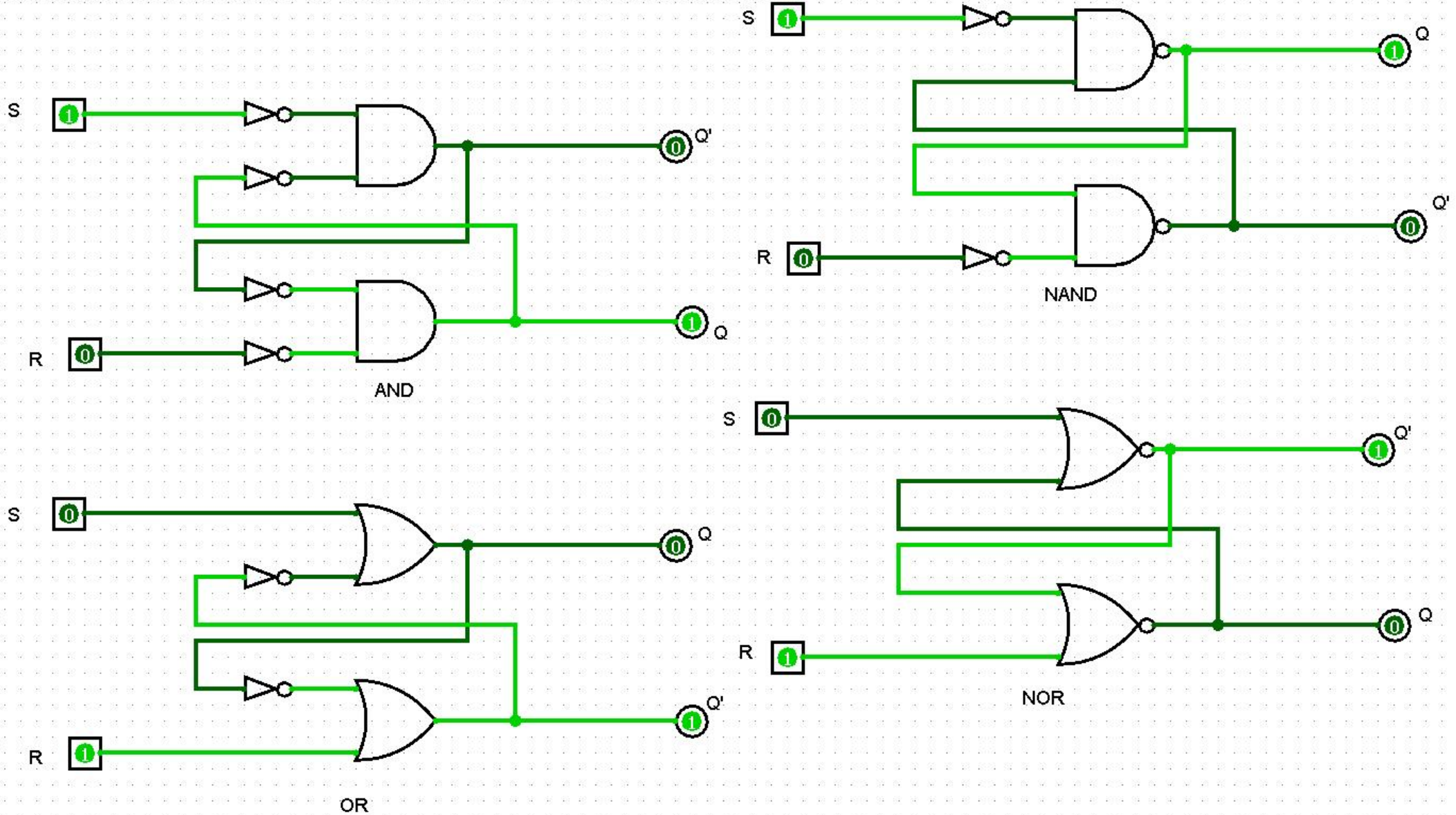D LATCH OR GATED LATCHES WITH DIFFERENT GATES CAN BE APPLIED IN A SIMILAR WAY




Gated SR Latch

 - A Gated SR latch (clocked SR Latch) is a SR latch with enable input which works when enable is 1 and retain the previous state when enable is 0.



E	S	R	Q	\bar{Q}
0	0	0	latch	latch
0	0	1	latch	latch
0	1	0	latch	latch
0	1	1	latch	latch
1	0	0	latch	latch
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

 


S	R	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

Characteristics Equation for SR Flip Flop: $Q_{N+1} = Q_N R' + S$

D Flip-Flop

 D flip-flop operates with only positive clock transitions or negative clock transitions. Whereas, D latch operates with enable signal. That means, the output of D flip-flop is insensitive to the changes in the input, D except for active transition of the clock signal.




Q	D	$Q_{(t+1)}$
0	0	0
0	1	1
1	0	0
1	1	1

Characteristics Equation for D Flip Flop: $Q_{t+1} = D$

JK Flip-Flop

 JK flip-flop is the modified version of SR flip-flop. It operates with only positive clock transitions or negative clock transitions.




J	K	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristics Equation for JK Flip Flop: $Q_{N+1} = JQ_N' + K'Q_N$

T Flip-Flop

 T flip-flop is the simplified version of JK flip-flop. It is obtained by connecting the same input 'T' to both inputs of JK flip-flop. It operates with only positive clock transitions or negative clock transitions.




T	Q_N	Q_{N+1}
0	0	0
0	1	1
1	0	1
1	1	0

Characteristics Equation for JK Flip Flop: $Q_{N+1} = TQ_N' + T'Q_N = T \oplus Q_N$


Conversion for Flip-Flops

EXCITATION TABLE




Q_N	Q_{N+1}	S	R	J	K	D	T
0	0	0	X	0	X	0	0
0	1	1	0	1	X	1	1
1	0	0	1	X	1	0	1
1	1	X	0	X	0	1	0

Edge-Triggered D Flip-Flop

 


 
- $CP = 0 \Rightarrow S \text{ \& } R = 1 \Rightarrow \text{STEADY STATE OUTPUT}$
- $D = 0 \text{ \& } CP = 1 \Rightarrow S = 1, R = 0 \Rightarrow Q = 0$
- $D = 1 \text{ \& } CP = 1 \Rightarrow S = 0, R = 1 \Rightarrow Q = 1$




Edge-Triggered SR Flip-Flop

 - To adjust the clocked RS latch for edge triggering, we must actually combine two identical clocked latch circuits, but have them operate on opposite halves of the clock signal.
- The edge-triggered SR NAND flip-flop is shown below.



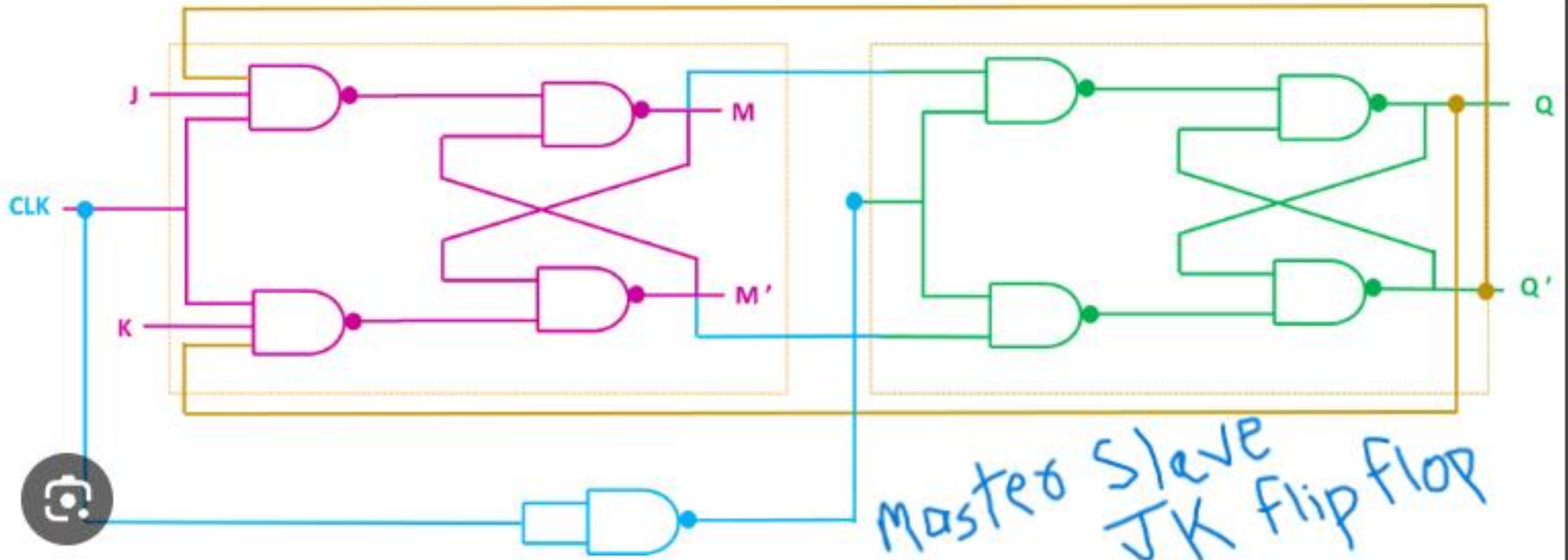


4-bit shift register using d flip flop

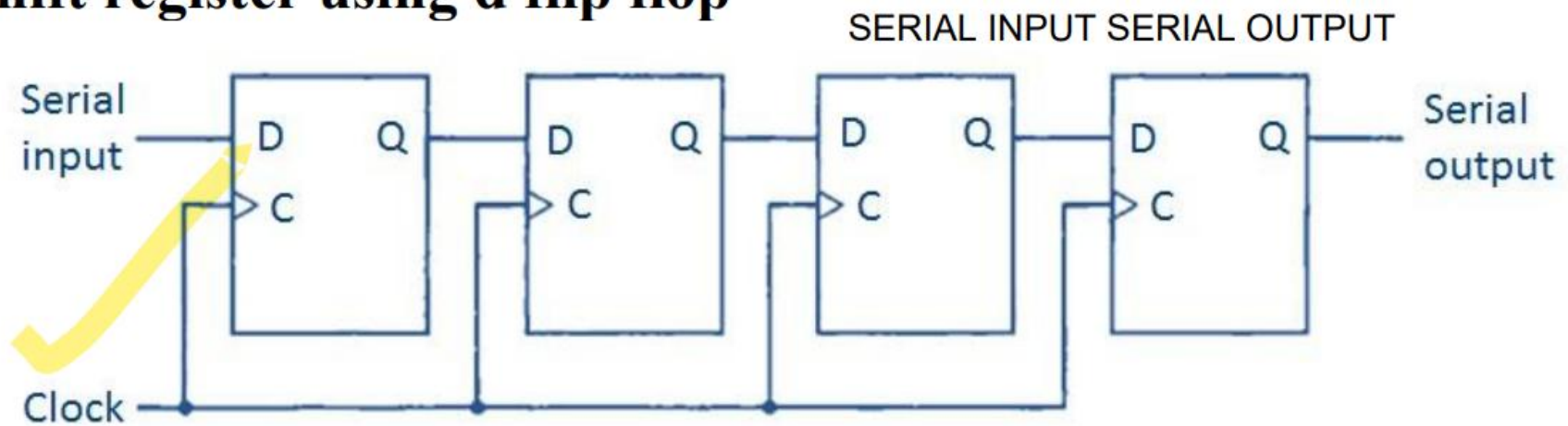


Serial-In Serial-Out Shift Register (SISO)

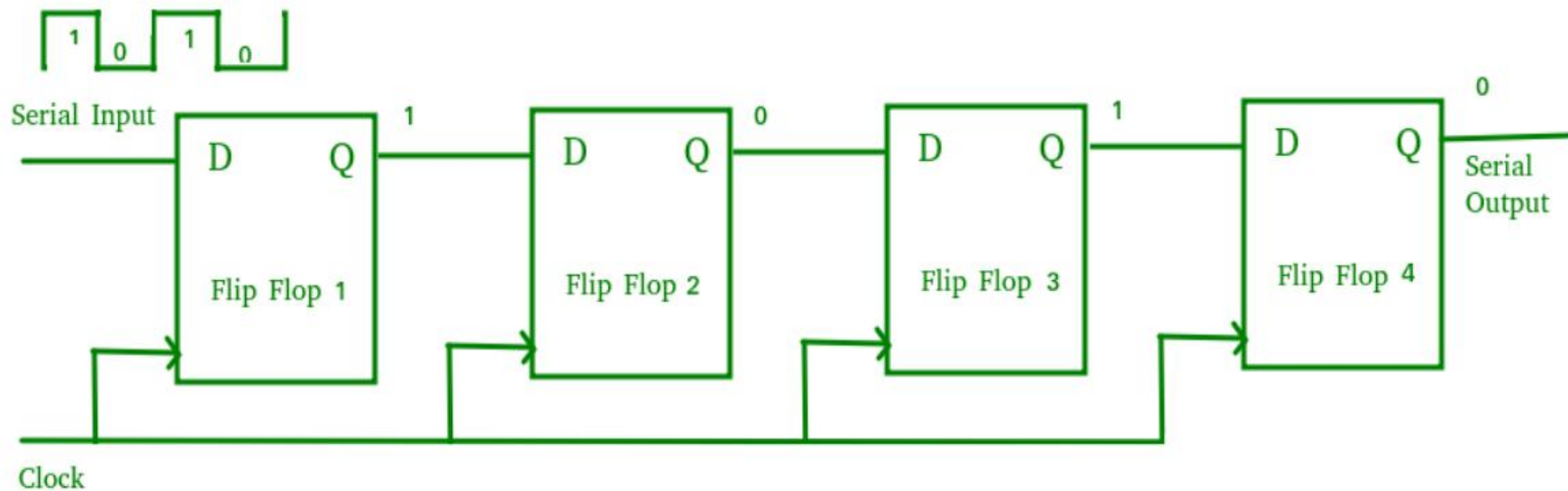- The shift register, which allows serial input (one bit after the other through a single data line) and produces a serial output is known as a Serial-In Serial-Out shift register.
- Since there is only one output, the data leaves the shift register one bit at a time in a serial pattern, thus the name Serial-In Serial-Out Shift Register.
- The main use of a SISO is to act as a delay element.




Serial-In Parallel-Out Shift Register (SIPO)

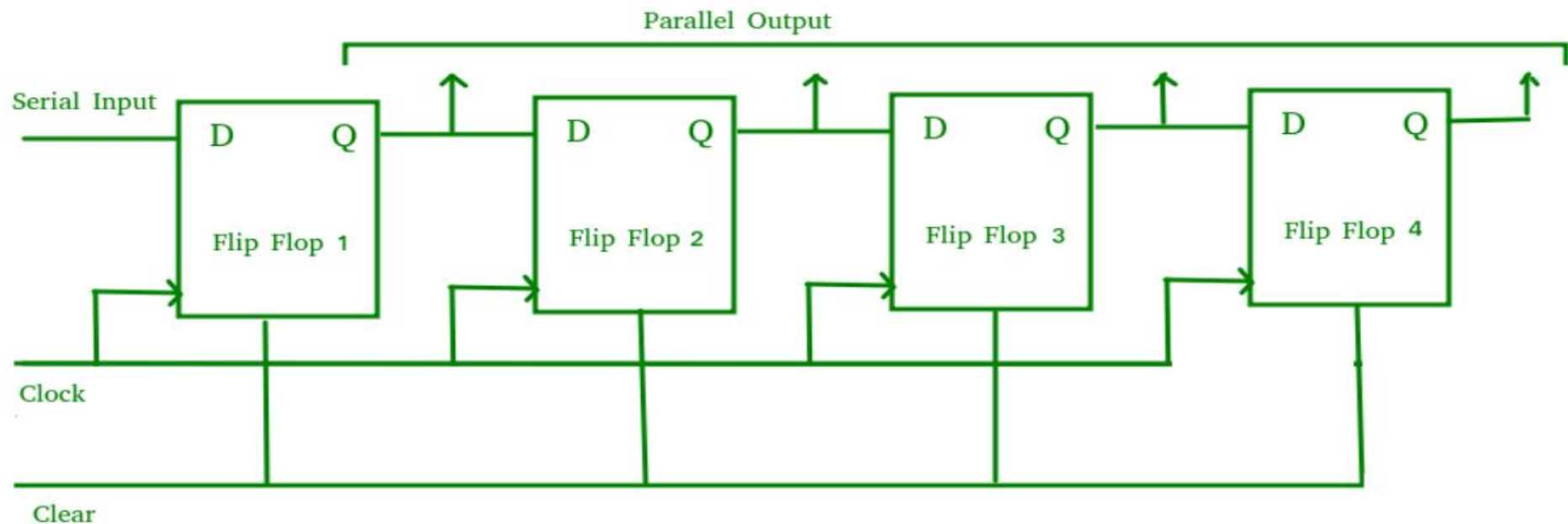- The shift register, which allows serial input (one bit after the other through a single data line) and produces a parallel output is known as the Serial-In Parallel-Out shift register
- Used in communication lines where demultiplexing of a data line into several parallel lines is required because the main use of the SIPO register is to convert serial data into parallel data.




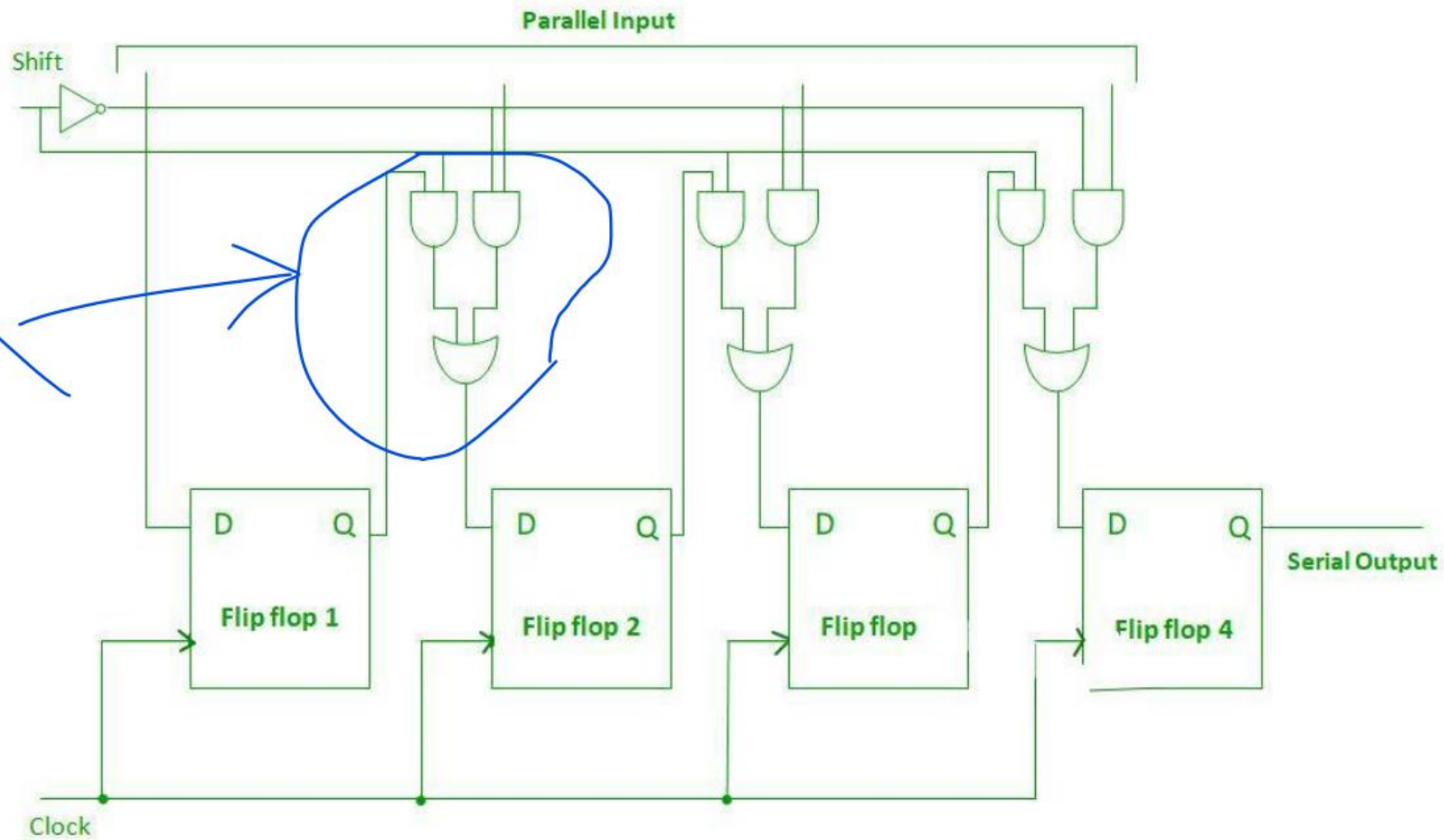Parallel-In Serial-Out Shift Register (PISO)




Parallel-In Parallel-Out Shift Register (PIPO)

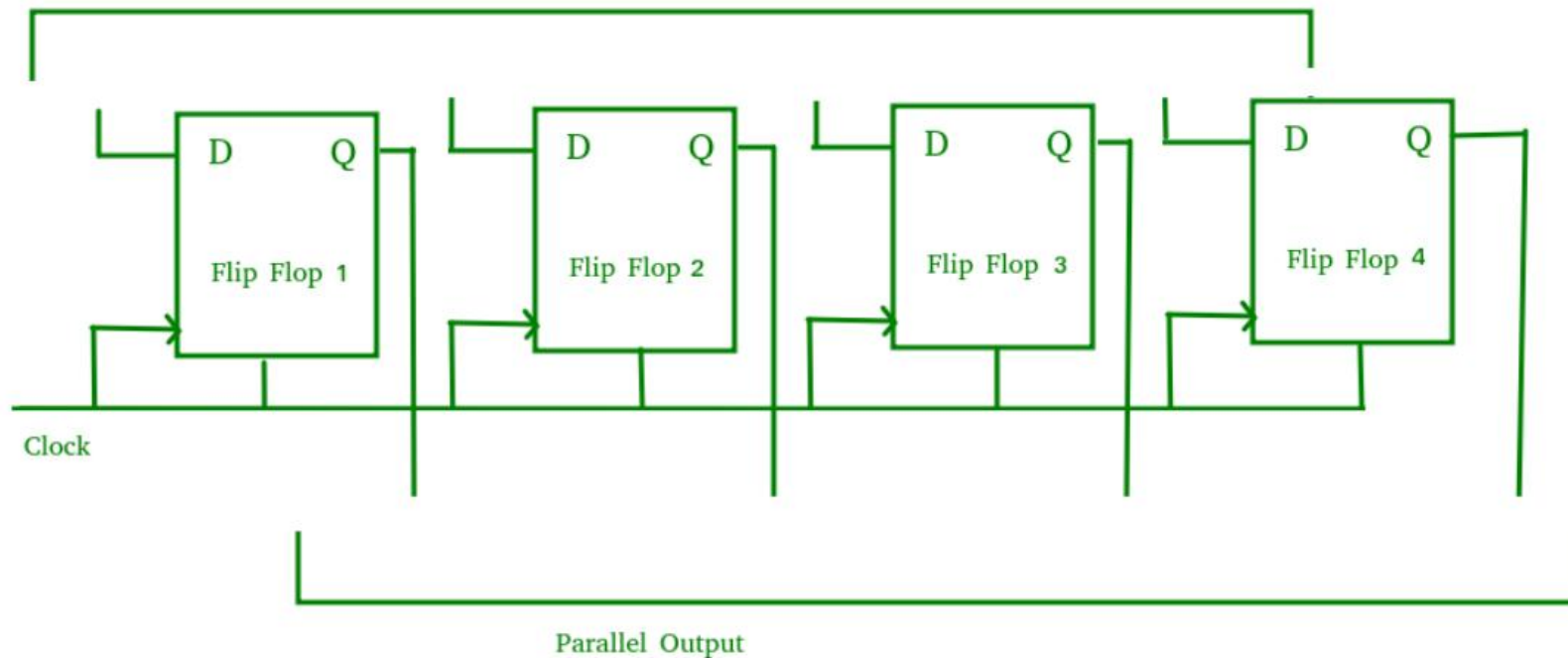
- The shift register, which allows parallel input and also produces a parallel output is known as Parallel-In parallel-Out shift register.
- A Parallel in Parallel out (PIPO) shift register is used as a temporary storage device and like SISO Shift register it acts as a delay element.



Bidirectional Shift Register

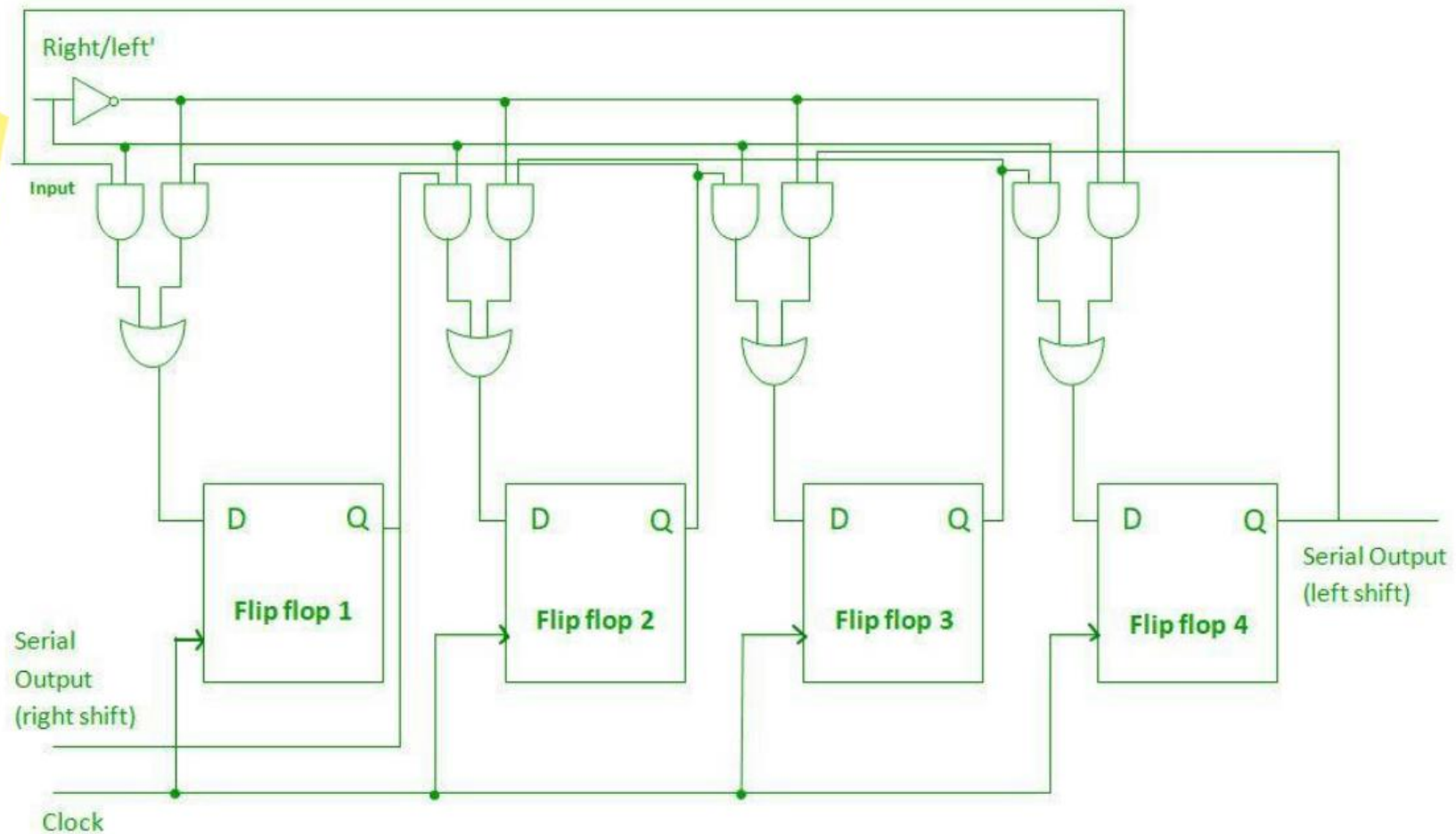



Universal Shift Register

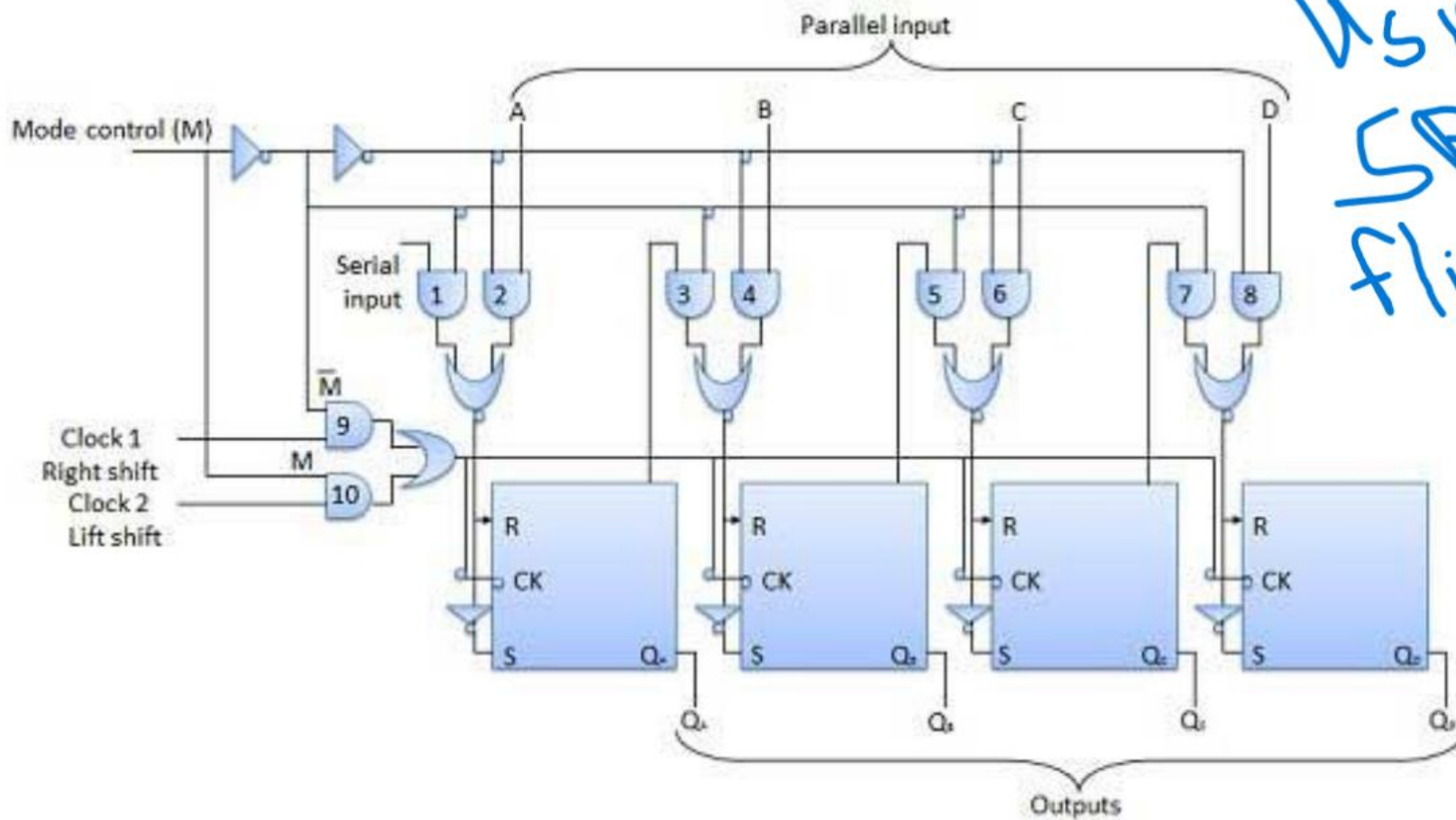

Universal Shift Register

USING D FLIPFLOP

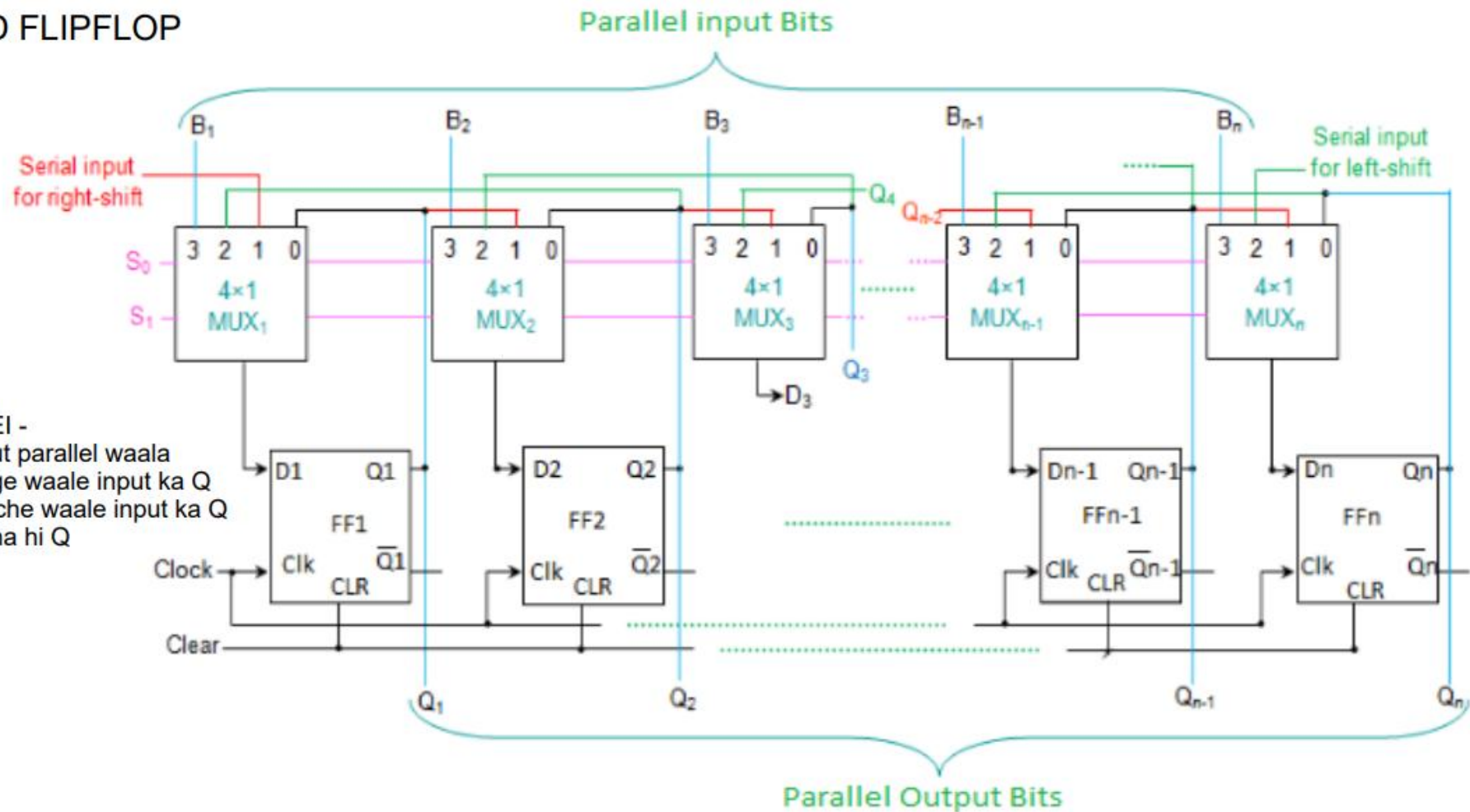

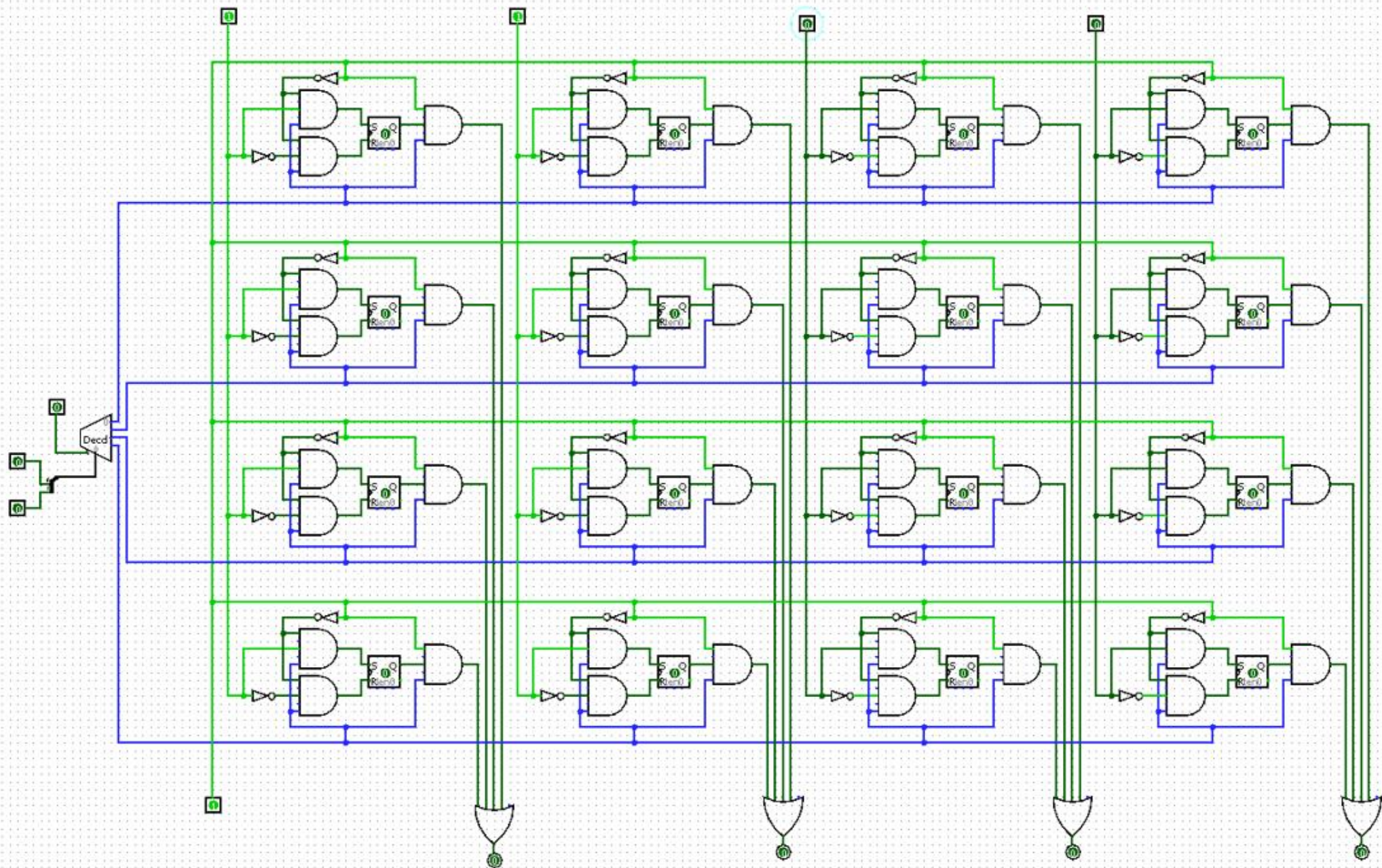



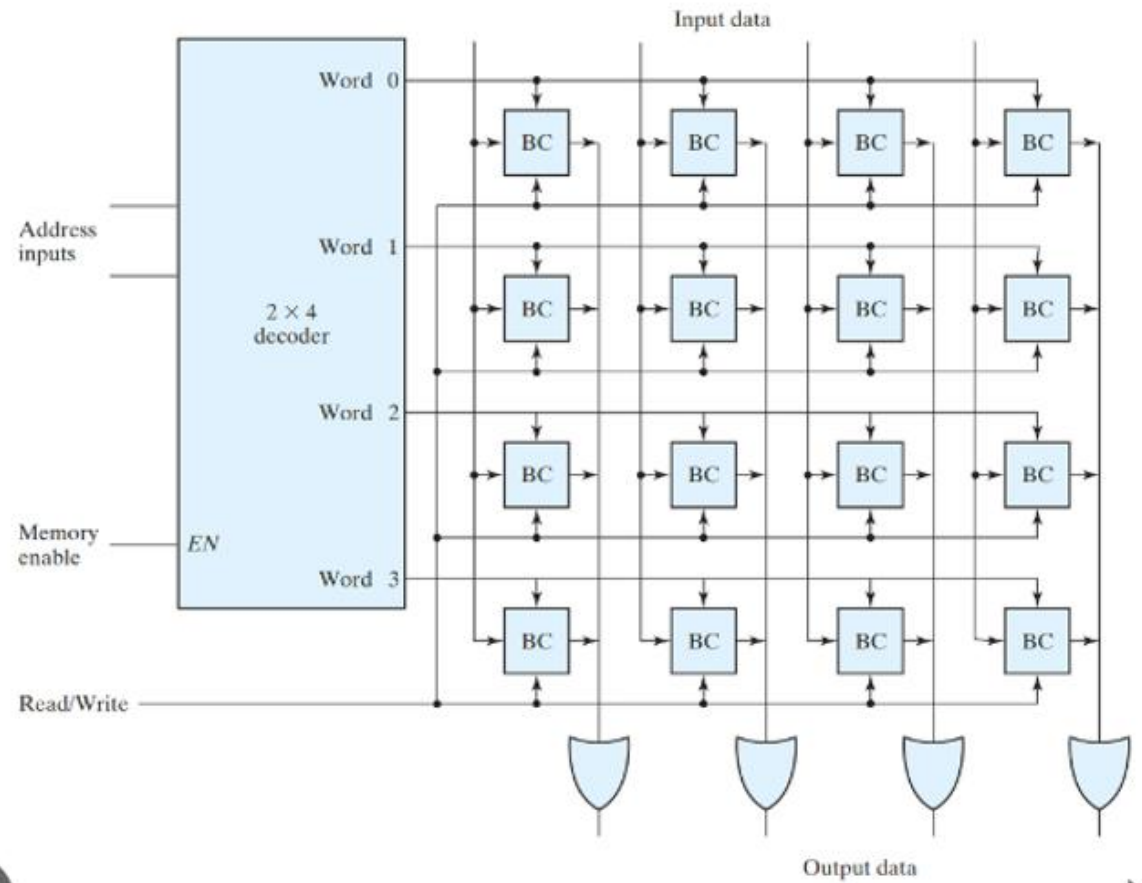
 


FIGURE 7.6
Diagram of a 4x4 RAM

 

Raspberry Pi

 

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


1,988 x 67

Building a Half Adder | Coding projects for kids and teens

Visit >


$$D = \bar{A}.B + A.\bar{B}$$

$$B_o = \bar{A}.B$$

 


A	B	D	B _o
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Half Subtractor

 


Full Subtractor Circuit

 

2,521 × 1,419

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 


Inputs			Outputs	
A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full-adder circuit diagram and truth table, where A , B , and C in are... | Download Scientific Diagram


Visit >

Ripple Carry Adder

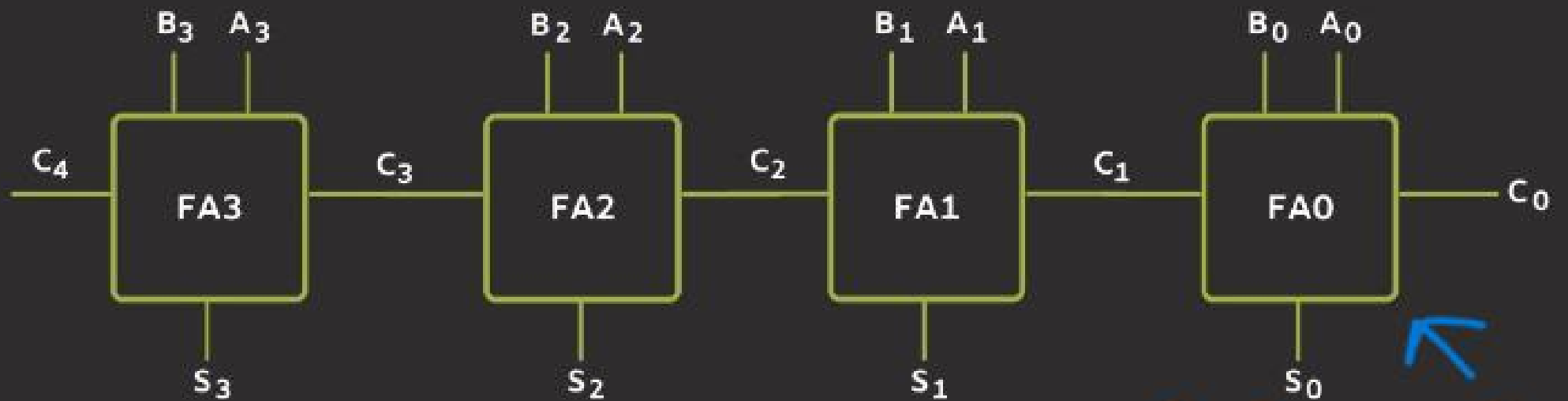

Ripple Carry Adder Explained (with Solved Example) |
Working and Limitation of Ripple Carry Adder

Watch >

 

To understand carry look ahead adder - <https://www.geeksforgeeks.org/carry-look-ahead-adder/>

